

# More on Sequential Logic

# Intro to Finite State Machines

**CS 64: Computer Organization and Design Logic**

**Lecture #16**

**Fall 2019**

Ziad Matni, Ph.D.


Dept. of Computer Science, UCSB

# THIS IS WHAT LEARNING LOGIC GATES FEELS LIKE

SEE, YOU JUST CONNECT THIS 12 INPUT REVERSE FLIP-FLOP TO THE CONTROLLED TWO-THIRDS ADDER, WHICH RESETS THE LATCHES IN THE NOT-NAND RELAY ARRAY, THEN LOOP BACK TO ODD-NUMBER INPUTS AND REVERSE ALL YOUR SWITCHES!

AND WHAT'S THAT DO?

SUBTRACTION.

 

# Administrative

---

- Lab 8 due Wednesday!

# Lecture Outline

---

- Exercises with Sequential Logic
- Introduction to Finite State Machines
  - Types
  - Examples
  - Exercises

# FINAL IS COMING!

- Tuesday, DEC. 10<sup>th</sup> in this classroom
- Starts at **12:00 PM \*\*SHARP\*\***
- Please start arriving 10 minutes early
- Please bring your UCSB IDs with you
- Closed book: no calculators, no phones, no computers



**STUDY GUIDE  
NOW ONLINE!**


# What's on the Final

---

- Everything

# Exercise 1

Given this circuit diagram:

 

- Write a logic function that describes the diagram in a “sum-of-product” format.
- Construct the truth table for this circuit
- Further optimize the logic function based a K-Map

# Exercise 2

---

- Let's design a 3-bit counter using D-FFs and logic gates.
- What's needed:
  - This counts  $000 \rightarrow 001 \rightarrow 010 \rightarrow \dots \rightarrow 111 \rightarrow 000$ 
    - i.e. from 0 to 7 and then loops again to 0, etc...
- Draw the T.T. based on this description
  - How many inputs? How many outputs?
  - Figure out what the “next states” look like based on “current states”
- Draw K-Maps and find optimal output functions





If a **combinational logic** circuit is an implementation of a ***Boolean function***,


then a **sequential logic** circuit can be considered an implementation of a ***finite state machine***.

# Finite State Machines (FSM)

- A **State** = An output or collection of outputs of a digital “machine”
- A **Machine** = A computational entity that predictably works based on one or more input conditions and yields a logical output
- A Finite State Machine: An **abstract machine** that can be in **exactly one** of a **finite** number of states at any given time

 
# Finite State Machines (FSM)

- The FSM can change from one state to another in **response to some external inputs**
- The change from one state to another is called a **transition**.



- An FSM is defined by a **list of its states**, its **initial state**, and **the conditions for each transition**.
- In CPUs, FSMs are widely used in the control unit

# Example of a Simple FSM: The Turnstile

 


## State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.

# Example of a Simple FSM: The Turnstile


This is called a  
*state diagram*

 


## State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.
Locked	Push	Locked	Nothing – you're locked! 😊
Unlocked	Coin	Unlocked	Nothing – you just wasted a coin! 😊
Unlocked	Push	Locked	When the customer has pushed through, locks the turnstile.

# General Form of FSMs

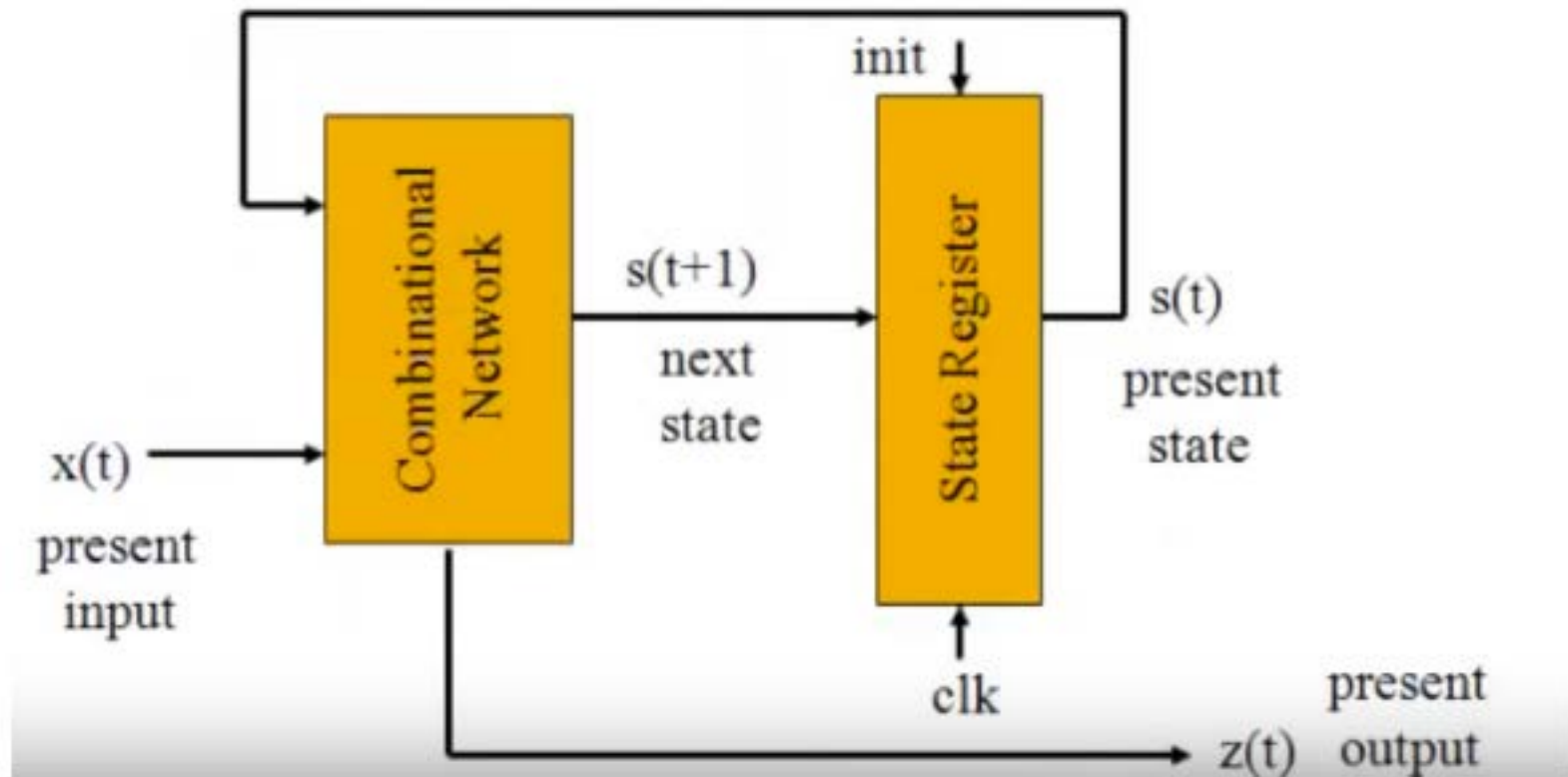

# Example

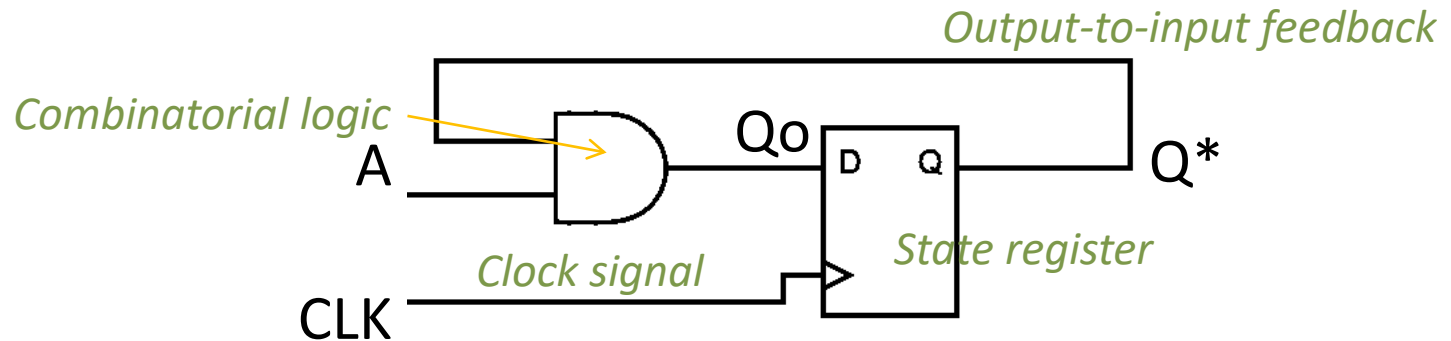

$$Q^* = Q_0 \cdot A$$

(read as: the next-state of Q will be  $Q_0 \cdot A$ )

i.e. ***On the next rising edge of the clock***, the output of the D-FF ( $Q^*$ ) will become the previous value of  $Q$  ( $Q_0$ ) **AND** the value of input  $A$



# FSM Types

---

**There are 2 types/models of FSMs:**

- **Moore machine**


- Output is function of present state only

- **Mealy machine**

- Output is function of present state *and* present input


# Moore Machine

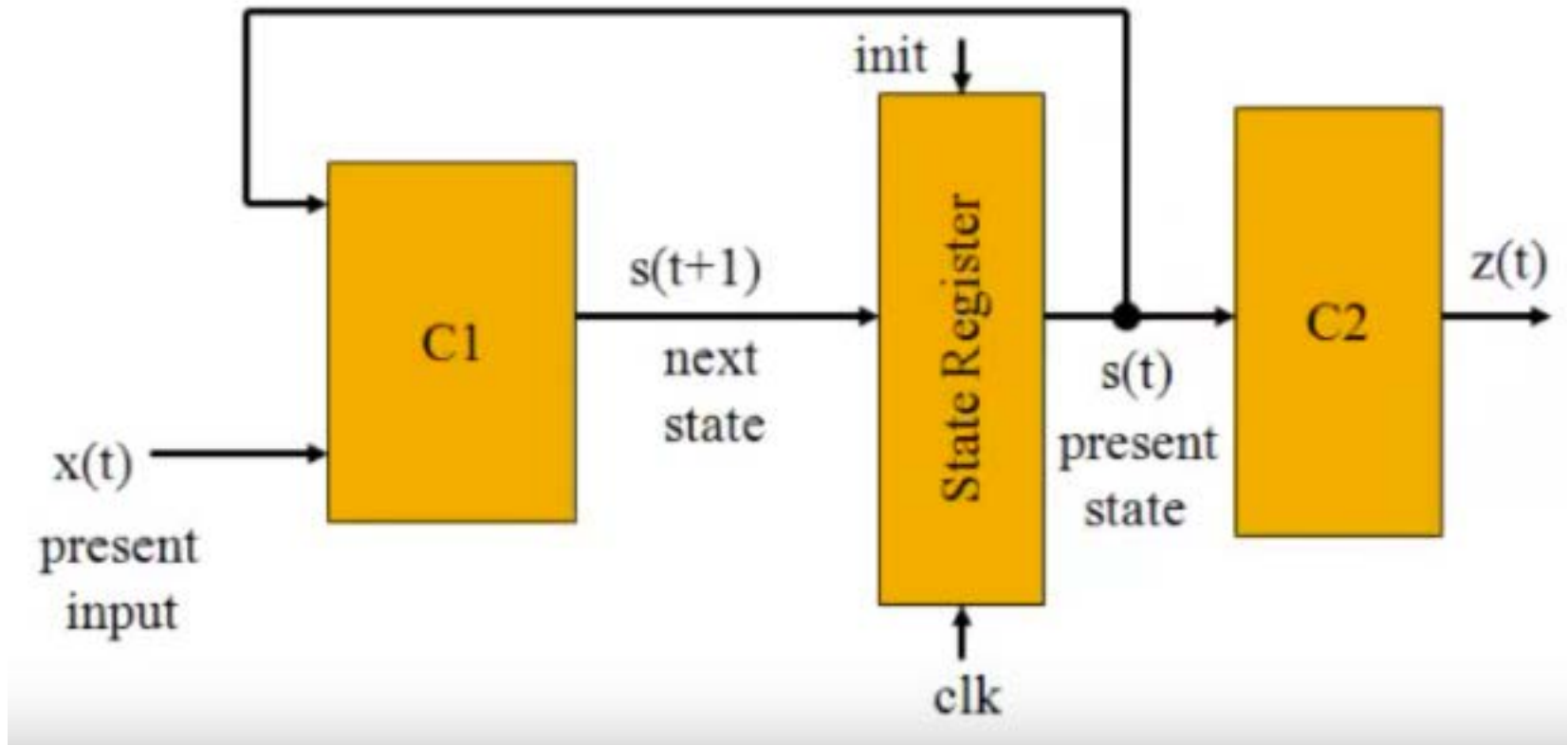***Output is a registered function of present state only***



# Example of a Moore Machine (*with 1 state*)

 ***Output is registered function of present state only***



$$Z = \overline{(Q^* + B)} = \overline{(Q_0 \cdot A + B)}$$


On the next rising edge of the clock, the output of the entire circuit (Z) will become

(the previous value of Q ( $Q_0$ ) **AND** the value of input A) **NOR** B

**NOTE:** CLK is NOWHERE IN THE EQUATION!!!

# Mealy Machine

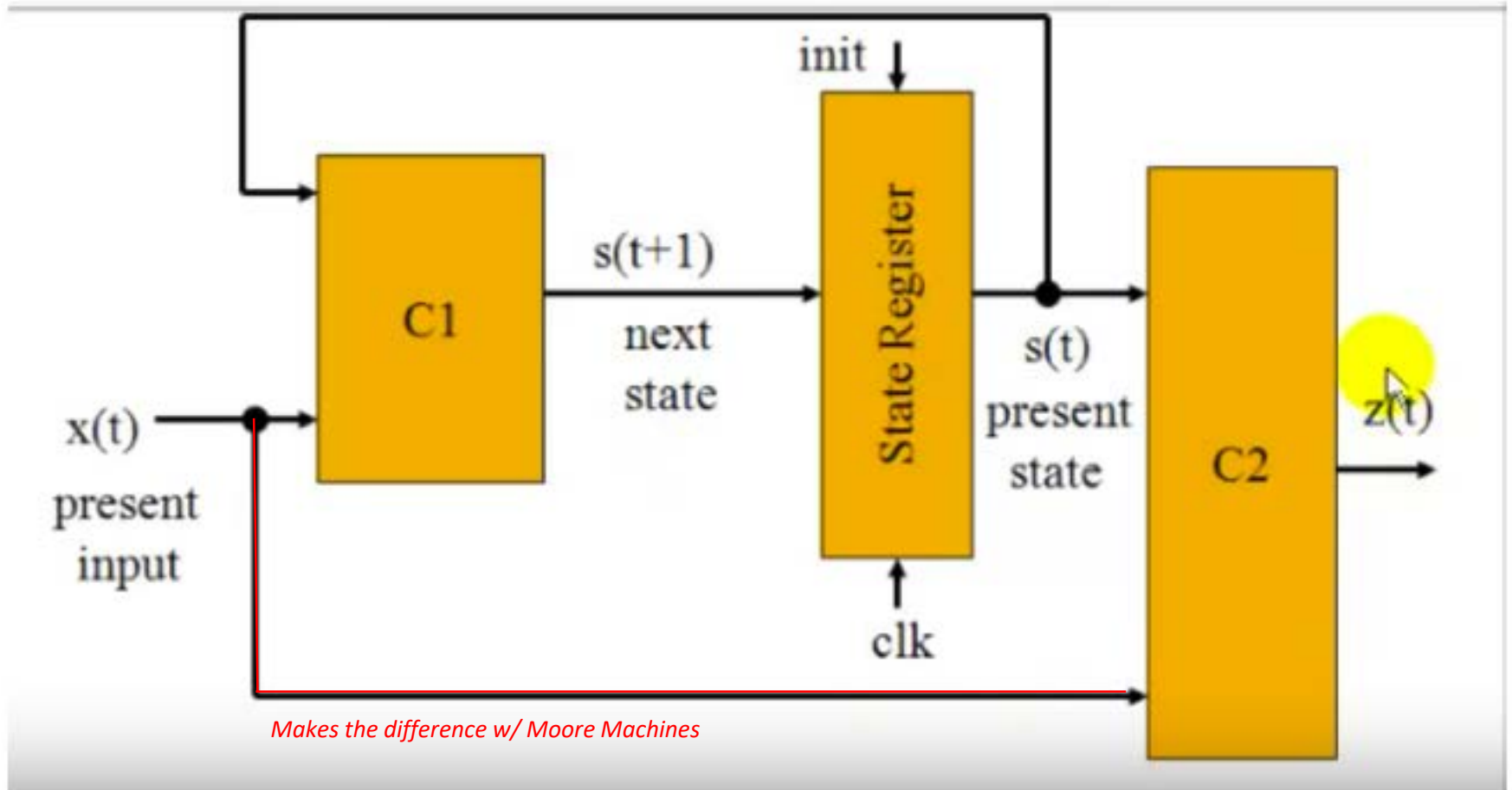***Output is a registered function of present state and present input***



# Example of a Moore Finite State Machine

## WASHER\_DRYER

- Let's “build” a sequential logic FSM that acts as a controller to a *simplistic* washer/dryer machine
- This machine takes in various inputs in its operation (we'll only focus on the following sensor-based ones):

*Coin is in (vs it isn't in)*

*Soap is present (vs it's used up)*

*Clothes are still wet (vs clothes are dry)*

- This machine also issues 1 output while running:

“Done” indicator

# Machine Design

---

- We want this machine to have **4 distinct states** that we go from one to the next in this sequence:

## 1. Initial State

- Where we are when we are waiting to start the wash

## 2. Wash


- Where we wash with soap and water

## 3. Dry


- Where we dry the clothes

## 4. Done

# State Diagram for Washer-Dryer Machine

 

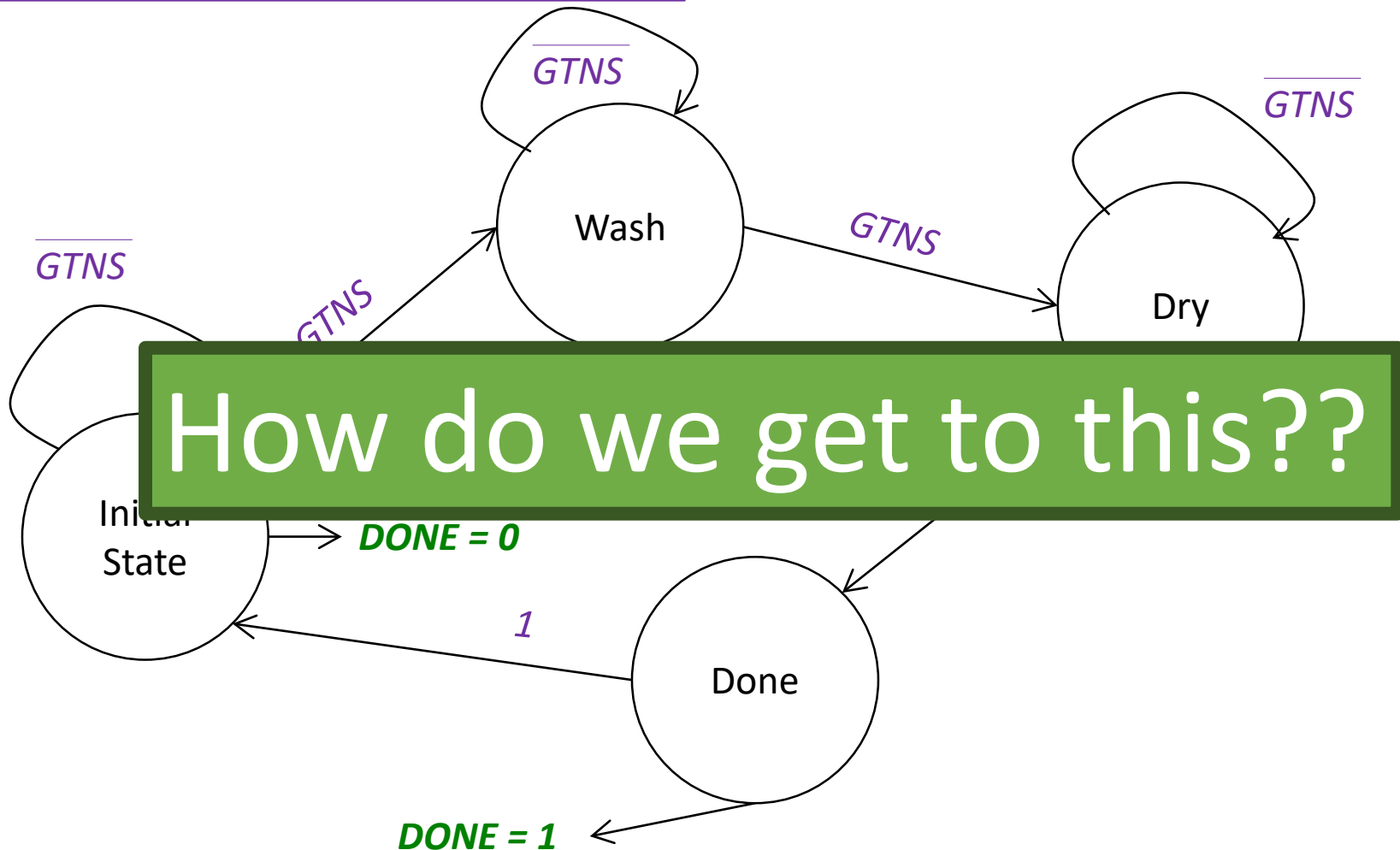$GTNS = COIN\_IN + NO\_SOAP + CLTHS\_DRY$



# Combining the Inputs

*Coin is in (vs it isn't in)*

*Soap is no longer detected (vs it's still there)*

*Clothes are now dry (vs clothes are still wet)*

- Let's create a variable called **GTNS** (i.e. Go To Next State)
- GTNS is 1 if **any** of the following is true:
  - Coin is in
  - Soap is no longer detected
  - Clothes are now dry
  - **I assume that these 3 inputs to be mutually exclusive**



# What's Going to Happen?

## 1/2

*Coin is in (vs it isn't in)*

*Soap is no longer detected (vs it's still there)*

*Clothes are now dry (vs clothes are still wet)*

- We start at an “**Initial**” state whenever we start up the machine
  - Let's also assume this stage is when you'd put in the soap and clothes
  - Once input “Coin is in” is 1, GTNS is now 1
  - This event triggers leaving the current state to go to the next state
- This is followed by the next state, “**Wash**”
  - “Coin inserted” is now 0 at this point (so GTNS goes back to 0)
  - While soap is still present, GTNS goes back to 0
  - When the input “Soap is no longer present” goes to 1, GTNS goes to 1
  - This event triggers leaving the current state to go to the next state

# What's Going to Happen?

## 2/2


*Coin is in (vs it isn't in)*

*Soap is no longer detected (vs it's still there)*


*Clothes are now dry (vs clothes are still wet)*

- This is followed by the next state, **“Dry”**
  - This new state sets an output that triggers a timer
  - The input “Soap is no longer present” goes to 0, so GTNS is 0 also
  - While the input “Clothes are now dry” is 0 , GTNS remains at 0 too
  - When the input “Clothes are now dry” is 1, GTNS changes to 1
  - This event triggers leaving the current state to go to the next state
- This is followed by the next and last state, **“Done”**
  - When you're here, you go back to the “initial” state
  - No inputs to consider: you do move this regardless

# State Diagram for Washer-Dryer Machine

 


 $GTNS = COIN\_IN + NO\_SOAP + CLTHS\_DRY$


 
# Unconditional Transitions

- Sometimes the transition is unconditional
  - Does not depend on any input –  
you go from **State X** to **State Y** regardless...
- We then diagram this as a “**1**” (for “always does this”)



# Representing The States

- How many bits do I need to represent all the states in this Washer-Dryer Machine?

- There are 4 unique states (including “init”)

- So, 2 bits

- If my state machine will be built using a memory circuit (most likely, a D-FF), how many of these should I have?

- 2 bits = 2 D-FFs

- There is another scheme to do this called “One Hot Method”

- Unfortunately, there’s no time to cover this method...

State	S1	S0
Initial	0	0
Wash	0	1
Rinse	1	0
Dry	1	1

# Example of a Moore FSM 2

## DETECT\_1101


- Let's build a sequential logic FSM that **always detects a specific serial sequence of bits: *1101***
- We'll start at an "Initial" state (S0)
- We'll first look for a **1**. We'll call that "State 1" (S1)
  - Don't go to S1 if all we find is a **0**!
- We'll then keep looking for another **1**. We'll call that "State 11" (S2)

# Example of a Moore Machine 2

## DETECT\_1101

- Then... a **0**. We'll call that "State 110" (S3)
- Then another **1**.  
We'll call that "State 1101"(S4) – this will also output a **FOUND** signal
- We will always be detecting "1101" (it doesn't end)  
So, as SOON as S4 is done, we keep looking for 1s or 0s
- Example: if the input stream is **111101110101101000011111011011**  
we detect "1101" at                   ↑    ↑           ↑                                   ↑    ↑

# State Diagram 2

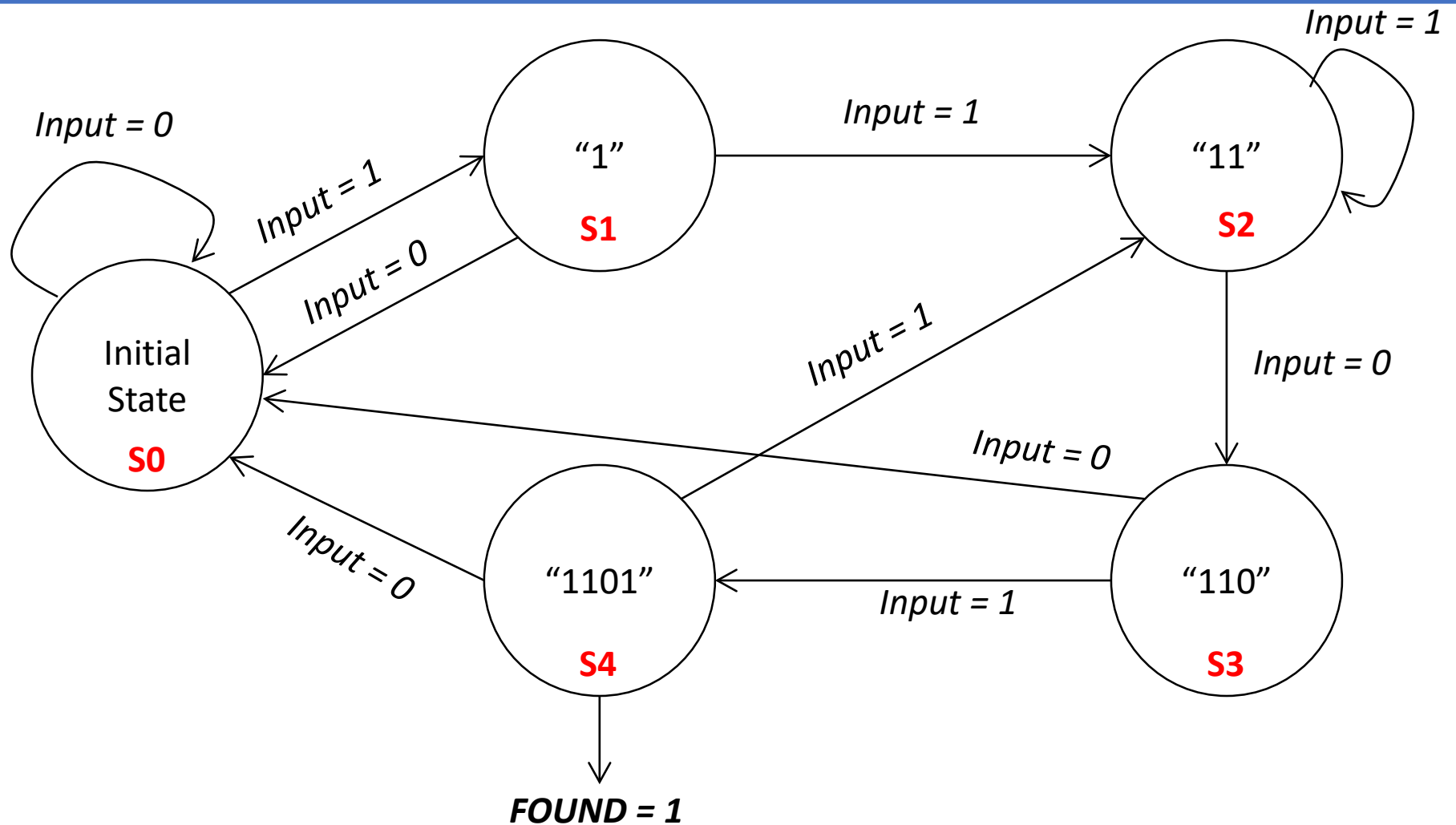



# Representing The States

- How many bits do I need to represent all the states in this “**Detect 1101**” Machine?
- There are 5 unique states (including “init”)
  - So, 3 bits
- How many D-FFs should I have to build this machine?
  - 3 bits = 3 D-FFs

State	B2	B1	B0
Initial	0	0	0
Found “1”	0	0	1
Found “11”	0	1	0
Found “110”	0	1	1
Found “1101”	1	0	0
N/A	1	0	1
	1	1	X

# Designing the Circuit for the FSM

---

## 1. We start with a T.T

- Also called a “State Transition Table”

## 2. Make K-Maps and simplify

- Usually give your answer as a “sum-of-products” form

## 3. Design the circuit

- Have to use D-FFs to represent the state bits

*Note: We are ignoring the N/A states*

# 1. The Truth Table (The State Transition Table)

CURRENT STATE				INPUT(S)	NEXT STATE			OUTPUT(S)
State	B2	B1	B0	I	B2*	B1*	B0*	FOUND
Initial	0	0	0	0	0	0	0	0
				1	0	0	1	0
Found "1"	0	0	1	0	0	0	0	0
				1	0	1	0	0
Found "11"	0	1	0	0	0	1	1	0
				1	0	1	0	0
Found "110"	0	1	1	0	0	0	0	0
				1	1	0	0	0
Found "1101"	1	0	0	0	0	0	0	1
				1	0	1	0	1

## 2. K-Maps for $B2^*$ and $B1^*$

State	B2	B1	B0	I	B2*	B1*	B0*	FOUND
Initial	0	0	0	0	0	0	0	0
				1	0	0	1	0
Found "1"	0	0	1	0	0	0	0	0
				1	0	1	0	0
Found "11"	0	1	0	0	0	1	1	0
				1	0	1	0	0
Found "110"	0	1	1	0	0	0	0	0
				1	1	0	0	0
Found "1101"	1	0	0	0	0	0	0	1
				1	0	1	0	1

You need to do this for all state outputs

- $B2^* = !B2.B1.B0.I$

- No further simplification

- $B1^* = !B2.!B1.B0.I + B2.!B1.!B0.I + !B2.B1.!B0$

**$B2^*$**

<b>B2.B1 B0.I</b>	00	01	11	10
00				
01				
11		<b>1</b>		
10				

**$B1^*$**

<b>B2.B1 B0.I</b>	00	01	11	10
00		<b>1</b>		
01		<b>1</b>		<b>1</b>
11	<b>1</b>			
10				

## 2. K-Map for $B0^*$

Output FOUND

- $B0^* = !B2.!B1.!B0.I$   
 $+ !B2.B1.!B0.!I$

$B0^*$

<b>B2.B1 B0.I</b>	00	01	11	10
00		1		
01	1			
11				
10				

- FOUND =  $B2.!B1.!B0$ 
  - Note that FOUND does not need a K-Map. It is always “1” (i.e. True) when we are in state S4 (i.e. when  $B2=1, B1=0, B0=0$ )


### 3. Design the Circuit

Note that CLK is the input to ALL the D-FFs' clock inputs. This is a *synchronous machine*.

Note the use of labels (example: B2 or B0-bar) instead of routing wires all over the place!

Note that I issued both  $B_n$  and  $B_n$ -bar from all the D-FFs – it makes it easier with the labeling and you won't have to use NOT gates!

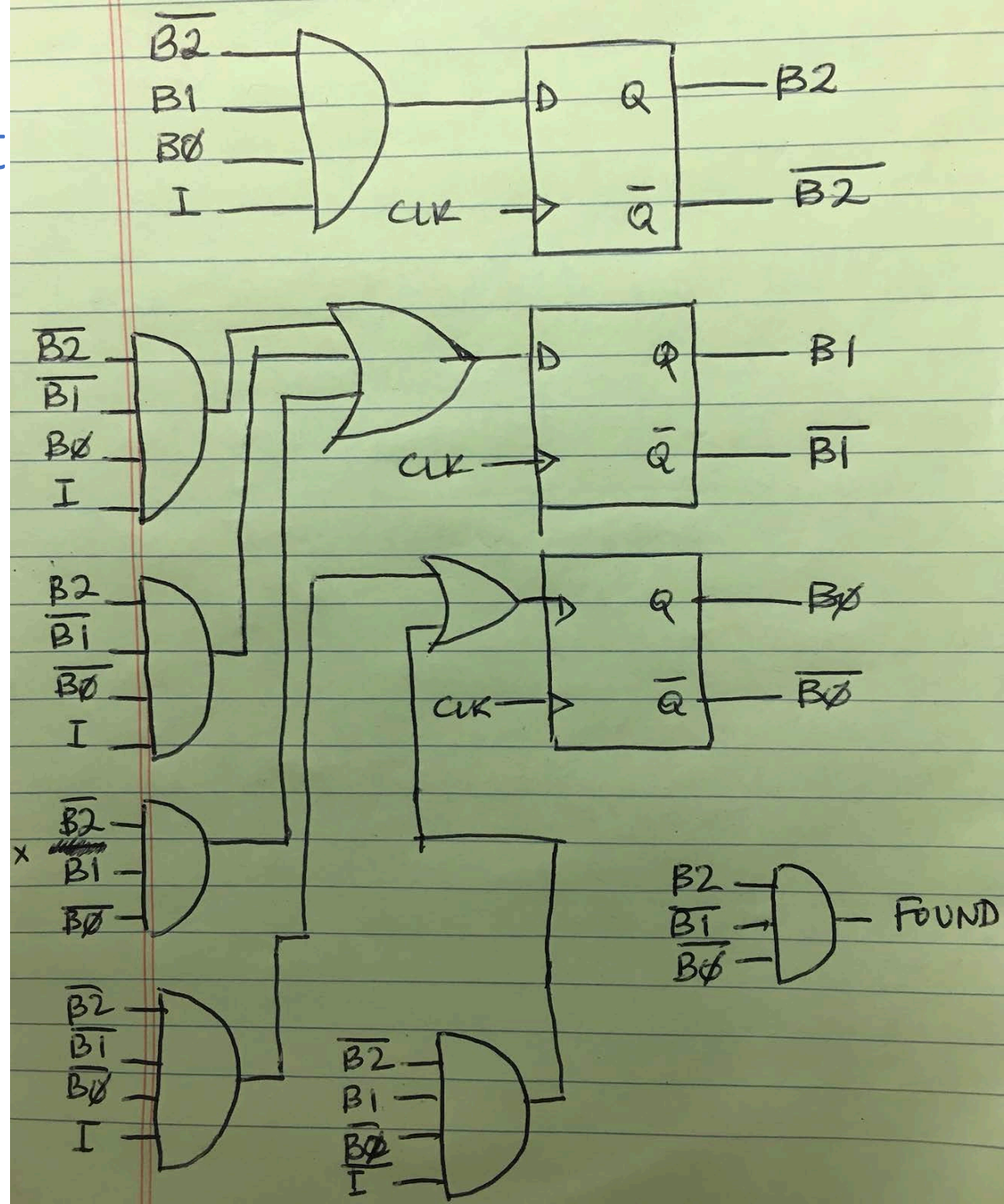Note that the sole output (FOUND) does **not** need a D-FF because it is **NOT A STATE BIT!**



# YOUR TO-DOs

---

- Review this FSM stuff!
- Finish Lab #8!

**</LECTURE>**