

# Simplification of Combinatorial Digital Logic

**CS 64: Computer Organization and Design Logic**

**Lecture #13**

**Fall 2019**

Ziad Matni, Ph.D.


Dept. of Computer Science, UCSB

# This Week on “Didja Know Dat?!”


One of the first commercially available micro-processors (CPUs) was Intel’s 8008 in the early 1970s and its follow-up the 8080 (1976).

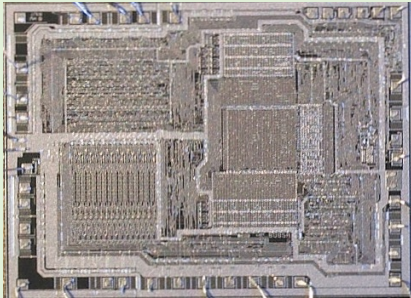**The 8080 is STILL in production!**



The size of the 8080 semiconductor (i.e. inside the ceramic package with all the pins) is  $4.2 \times 4.8 \text{ mm}^2$  ( $20.16 \text{ mm}^2$ )



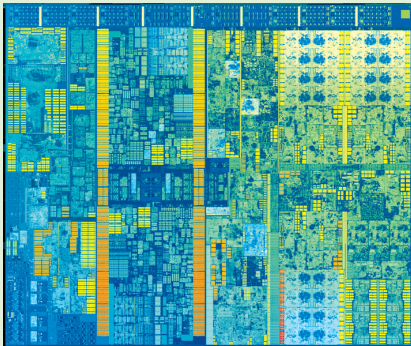By comparison, the Intel i7 Dual Core is  $9.2 \times 13.5 \text{ mm}^2$  ( $124.2 \text{ mm}^2$ )



**BUT THAT’S NOT A FAIR COMPARISON!**

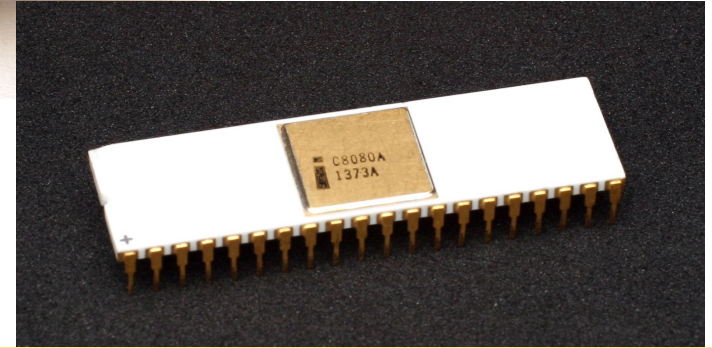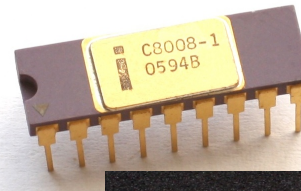

**8088:** 16-bit CPU.  
Cannot run Windows 1.0!

**i7 Core:** 64-bit CPUs.  
Have a TON more features.

*How do they do that?*


Moore’s Law

**The number of *transistors* on a microchip doubles every two years, though the cost of computers is halved.**

*More transistors means higher capabilities. Smaller transistors mean higher speeds.*
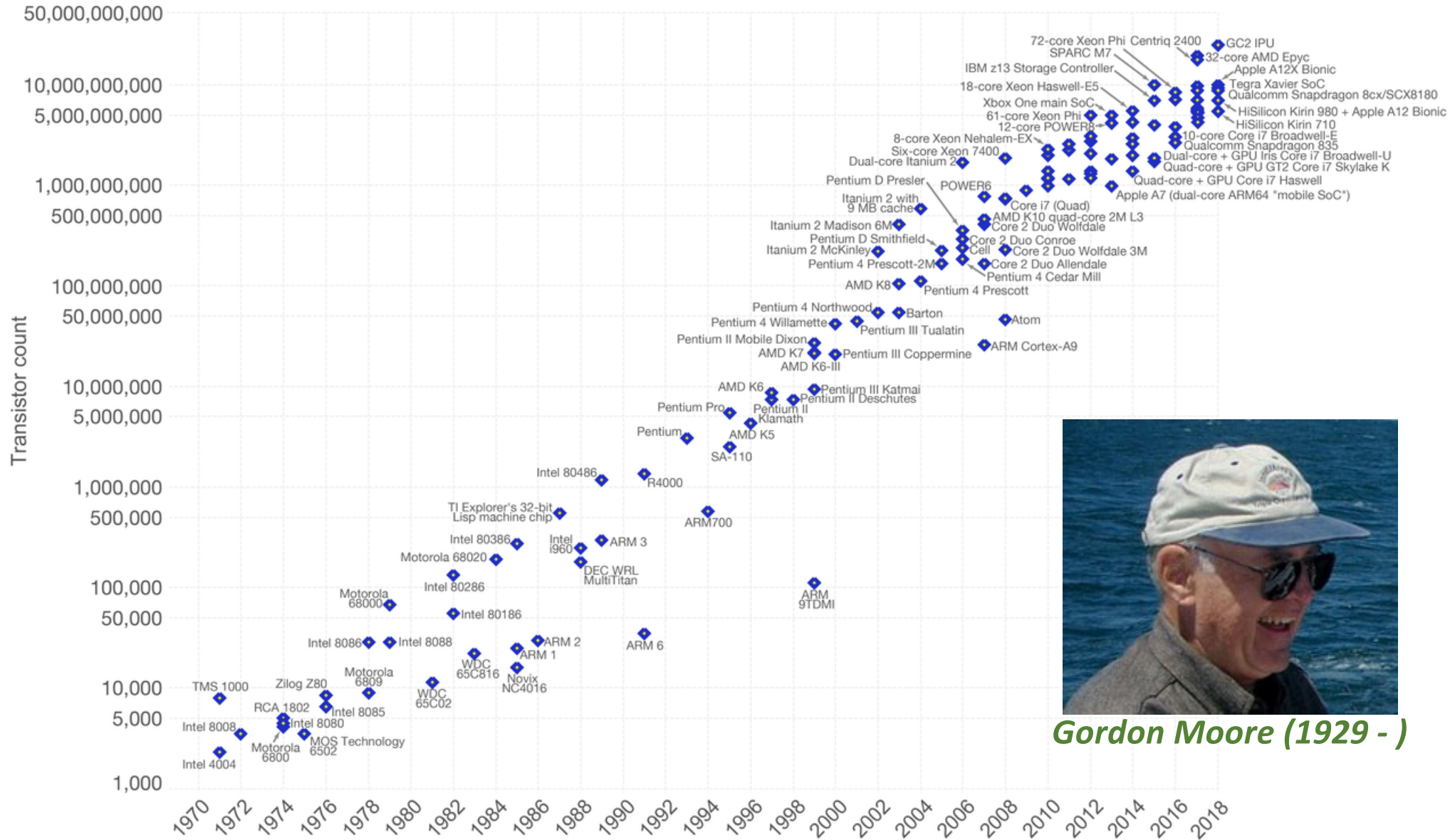
# Moore's Law – The number of transistors on integrated circuit chips (1971-2018)

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important as other aspects of technological progress – such as processing speed or the price of electronic products – are linked to Moore's law.



**Gordon Moore (1929 - )**

Data source: Wikipedia ([https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count))

The data visualization is available at [OurWorldinData.org](https://www.ourworldindata.org). There you find more visualizations and research on this topic.

Licensed under [CC-BY-SA](https://creativecommons.org/licenses/by-sa/4.0/) by the author Max Roser.

# Administrative

---

- Lab 6 due Wednesday
- You have 3 more labs after this...
- Midterm Exam Grades are On GauchoSpace

# Reviewing Your Midterm Exams

---

- You can review your midterm with a TA during office hours
  - *Last name: A thru M*      **Kunlong Liu**      **Tu 5 pm – 7 pm**
  - *Last name: N thru Z*      **Charlie Uslu**      **Tu 3 pm – 5 pm**
  - If you can't go to these o/hs, you can see me instead, but let me know ***many days ahead of time*** first so I can get your exam from the TA...
- When reviewing your exams:
  - Do **not** take pictures, do not copy the questions
  - TA cannot change your grade
    - If you have a legitimate case for grade change, the prof. will decide
    - Legitimate = When we graded, we added the total points wrong
    - Not legitimate = Why did you take off *N* points on this question????

# Lecture Outline

---

- Simplifying Binary Functions using **Karnaugh Maps**
- **Multiplexers**

# Digital Circuit Design Process

**CAN THIS PROCESS BE REVERSED?**

**Function  
definition**

**adder**



**Truth  
table**

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0




**Boolean  
expression**

$$\text{Sum} = (A\bar{B}) + (\bar{A}B)$$
$$\text{Carry} = AB$$



**Logic  
block**

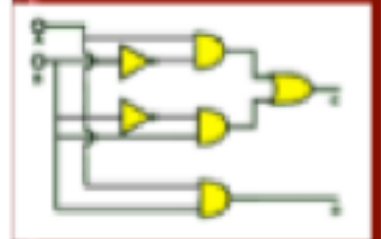



# Important: Laws of Binary Logic

**Circuit Equivalence** - each law has 2 forms that are duals of each other.

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$



# More Simplification Examples

---

Simplify the Boolean expression:

- $(A+B+C).!(D+E) + (A+B+C).(D+E)$

Simplify the Boolean expression and write it out on a truth table as proof

- $X.Z + Z.(!X + X.Y)$

Use DeMorgan's Theorem to re-write the expression below using at least one OR operation

- $\text{NOT}(X + Y.Z)$

# Scaling Up Simplification

---

- When we get to *more* than 3 variables, it becomes challenging to use truth tables
- We can instead use ***Karnaugh Maps*** to make it immediately apparent as to what can be simplified

# Example of a K-Map

	A	B	f(A,B)
0	0	0	a
1	0	1	b
2	1	0	c
3	1	1	d

B \ A	0	1
0	a	c
1	b	d

B \ A	0	1
0	0	2
1	1	3

A	B	f(A,B)
0	0	0
0	1	1
1	0	1
1	1	1

B \ A	0	1
0	0	1
1	1	1

# K-Maps with 3 or 4 Variables

$AB$		$A$			
		00	01	11	10
$C$	0	0	2	6	4
	1	1	3	7	5

*Note: In the original image, a blue bracket labeled 'B' is under the columns 01 and 11, and a blue bracket labeled 'C' is to the left of rows 0 and 1.*

$AB$		$A$			
		00	01	11	10
$CD$	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10



*Note: In the original image, a blue bracket labeled 'B' is under the columns 01 and 11, a blue bracket labeled 'C' is to the left of rows 11 and 10, and a blue bracket labeled 'D' is to the right of rows 01 and 11.*

Note the adjacent placement of:  
00 01 11 10



It's NOT:  
00 01 10 11

# Rules for Using K-Maps for Simplification

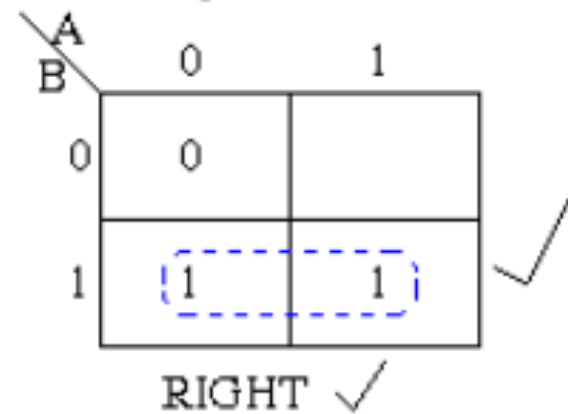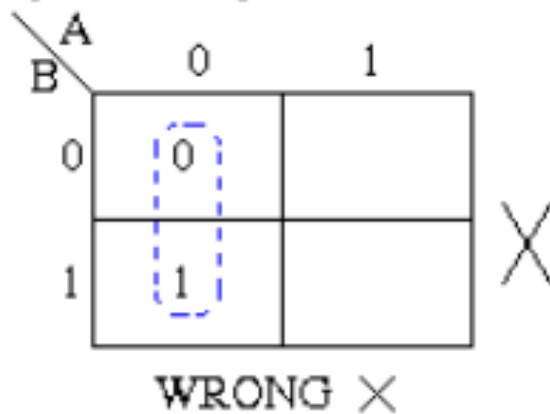1. Group together **adjacent cells** containing “1”
2. Groups should **not include** anything containing “0”



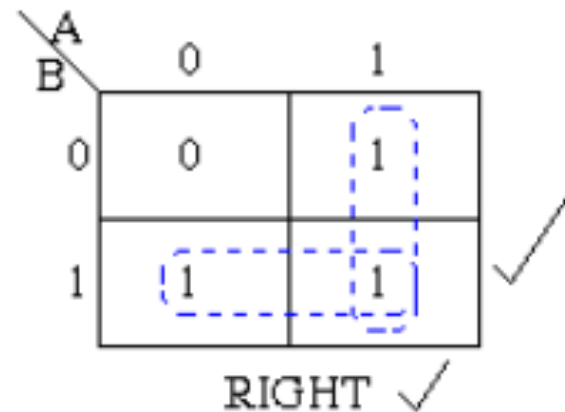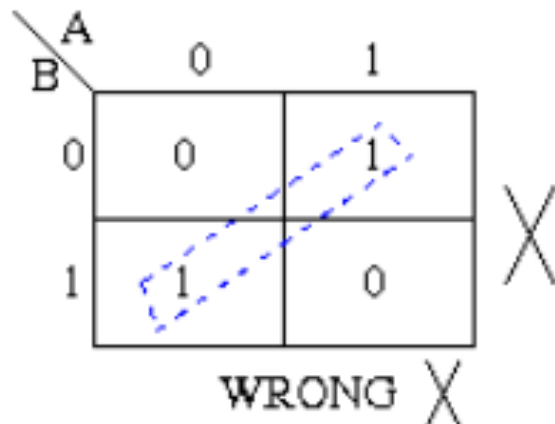3. Groups may be horizontal or vertical, but **not diagonal**



# Rules for Using K-Maps for Simplification

## 4. Groups must contain 1, 2, 4, 8, or in general $2^n$ cells.

<del>A</del> B	0	1
0	1	1
1	0	0

Group of 2

RIGHT ✓

<del>AB</del> C	00	01	11	10
0	0	1	1	1
1	0	0	0	0

Group of 3

WRONG ✗

<del>A</del> B	0	1
0	1	1
1	1	1

Group of 4

RIGHT ✓

<del>AB</del> C	00	01	11	10
0	1	1	1	1
1	0	0	0	1

Group of 5

WRONG ✗

# Rules for Using K-Maps for Simplification

## 5. Each group must be as large as possible

(Otherwise we're not being as minimal as we can be, even though we're not breaking any Boolean rules)

C \ AB	00	01	11	10
	0	1	1	1
0	1	1	1	1
1	0	0	1	1

RIGHT ✓


C \ AB	00	01	11	10
	0	1	1	1
0	1	1	1	1
1	0	0	1	1

WRONG ✗





# Rules for Using K-Maps for Simplification
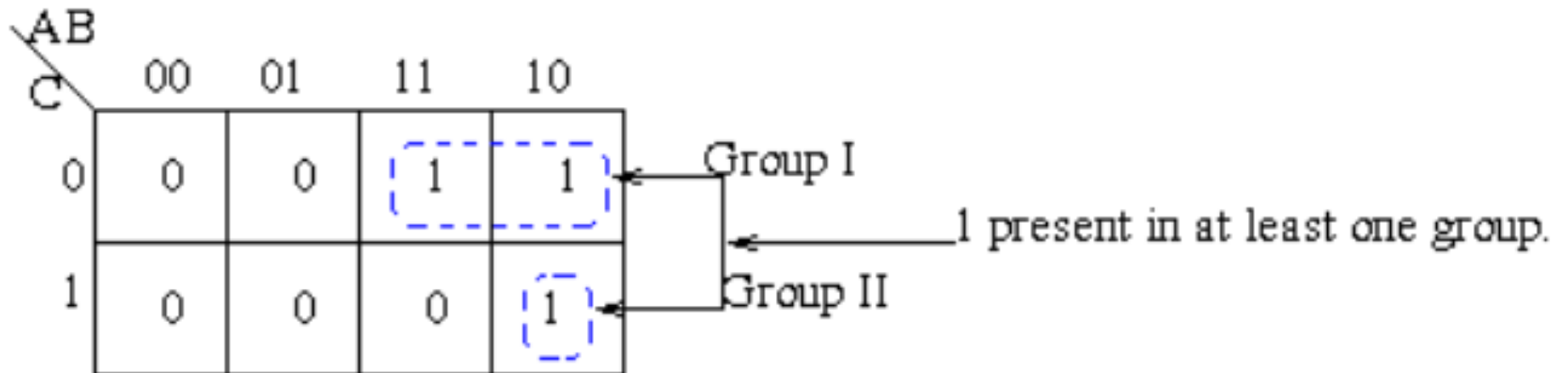
## 6. Each cell containing a “1” must be at least in one group



# Rules for Using K-Maps for Simplification

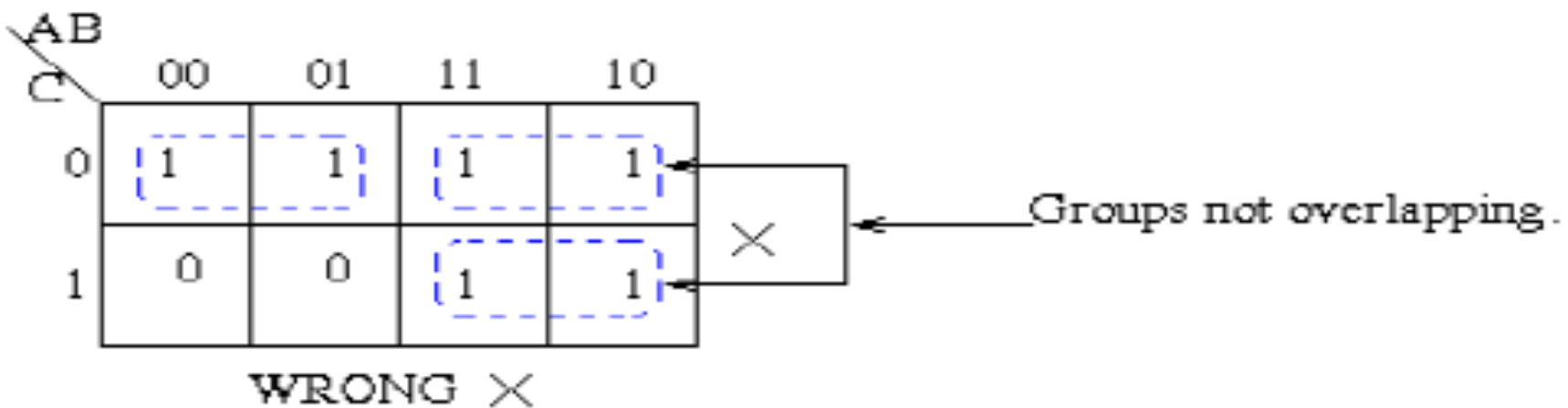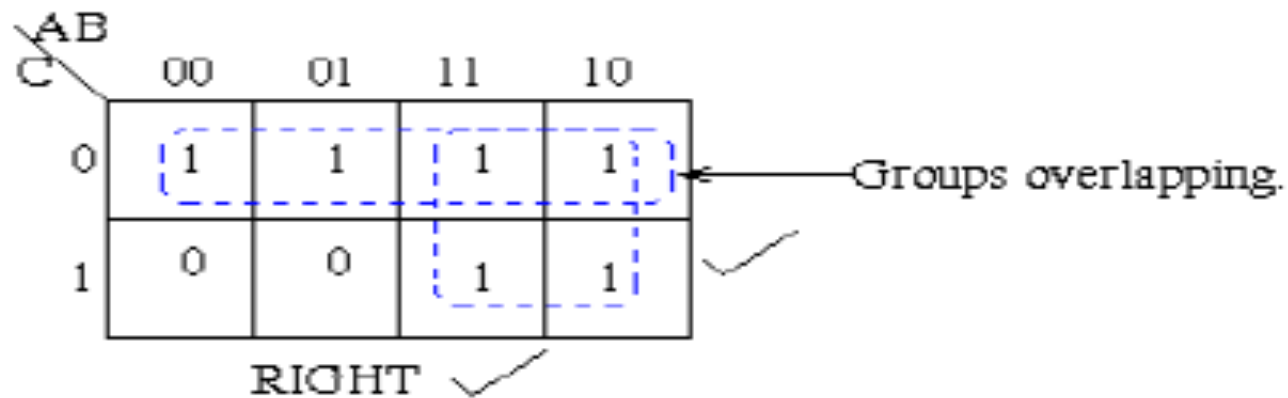
## 7. Groups may overlap esp. to maximize group size



# Rules for Using K-Maps for Simplification
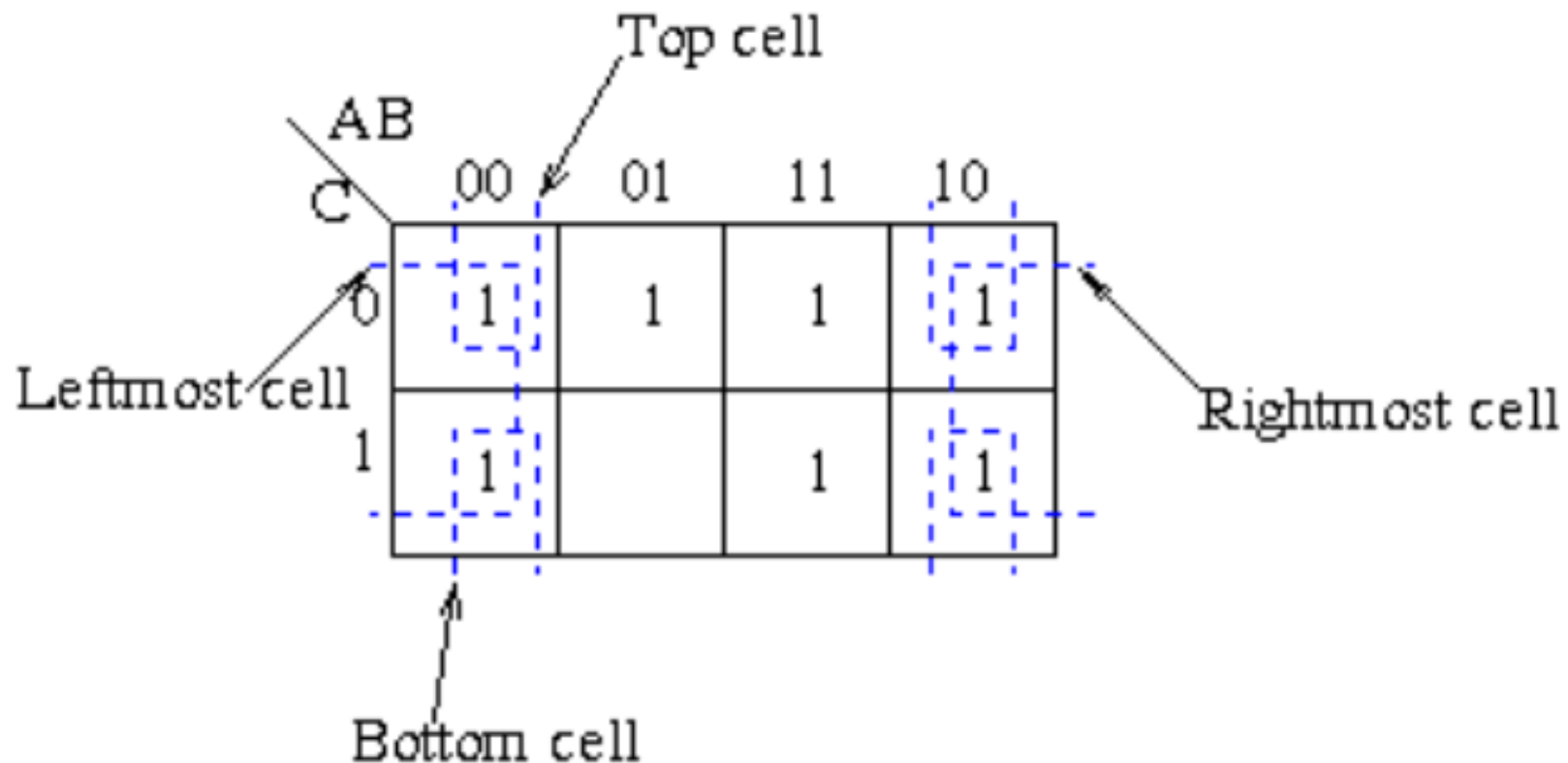
## 8. Groups may wrap around the table.

The leftmost cell in a row may be grouped with the rightmost cell and the top cell in a column may be grouped with the bottom cell.



## Example 1: 2 variables

$F(X,Y)$

$$= XY + Y$$

$$= Y(X + 1)$$

$$= Y$$

*Verifying results!*

$$F(X,Y) = Y$$

**Y = 1 column**

X \ Y	0	1
0		1
1		1

## Example 2: *3 variables*

$F(X,Y,Z)$

$$= XZ + Z(X' + XY)$$

$$= XZ + ZX' + ZXY$$

$$= Z(X + X' + XY)$$

$$= Z(1 + XY)$$

$$= Z$$

A Karnaugh map for the function F(X,Y,Z) with variables X, Y, and Z. The map is a 2x4 grid. The vertical axis is labeled Z, with values 0 and 1. The horizontal axis is labeled XY, with values 00, 01, 11, and 10. The cells for Z=0 are empty. The cells for Z=1 are all filled with the value 1. A red dashed rectangle encloses the four cells where Z=1. Above the map, a bracket labeled Y=1 spans the columns 01 and 11. Another bracket labeled X=1 spans the columns 11 and 10. A red arrow points from the text F(X,Y,Z) = Z to the red dashed box. A green dashed arrow points from the text Verifying results! to the same text.

	00	01	11	10
0				
1	1	1	1	1

*Verifying results!*

$$F(X,Y,Z) = Z$$

Example 3: *3 variables*

$$\neg A \neg B \neg C + \neg A \neg B C + \neg A B \neg C + \neg A B C + A \neg B \neg C + A \neg B C$$

		AB			
C		00	01	11	10
	0	1	1	1	1
	1	1	1		

$$F(X,Y,Z) = \neg C + \neg A$$

## Example 4: 4 variables

$$\begin{aligned}
 F(A,X,Y,Z) &= AX + Z(X+A'+Y) \\
 &= AX + ZX + ZA' + ZY
 \end{aligned}$$

$$F(A,X,Y,Z) = ZA' + AX + ZY$$

			$Y=1$	$X=1$
<b>AZ \backslash XY</b>				
	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>				
<b>01</b>		<b>1</b>	<b>1</b>	<b>1</b>
<b>11</b>		<b>1</b>	<b>1</b>	<b>1</b>
<b>10</b>			<b>1</b>	<b>1</b>



Example 4:      *4 variables*

$$F(A,B,C,D) = ABCD' + ABC'D + CD + A'B' + C'D$$

$$F(A,B,C,D) = A'B' + D + A\bar{B}C$$

Karnaugh map for the function  $F(A, B, C, D) = A + B + C + D$ . The map shows the function value (0 or 1) for all combinations of inputs A, B, C, and D. The function is 1 for all combinations where A=1, B=1, C=1, or D=1.

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	1	0	1	0

Groupings for the function  $F(A, B, C, D) = A + B + C + D$ :

- $B = 1$  (Grouping the columns where B=1, i.e., columns 01 and 11)
- $A = 1$  (Grouping the columns where A=1, i.e., columns 11 and 10)
- $D = 1$  (Grouping the rows where D=1, i.e., rows 01 and 11)
- $C = 1$  (Grouping the rows where C=1, i.e., rows 11 and 10)

# K-Map Rules Summary

---

1. Groups can contain only 1s
2. Only 1s in adjacent groups are allowed
3. Groups may ONLY be horizontal or vertical (no diagonals)
4. The number of 1s in a group must be a power of two (1, 2, 4, 8...)
5. Groups must be as large AND as few in no.s as “legally” possible
6. All 1s must belong to a group, even if it’s a group of one element
7. Overlapping groups are permitted
8. Wrapping around the map is permitted

# Exploiting “Don’t Cares”

---

- An *output variable* that’s designated “don’t care” (symbol = **X**) means that it could be a **0** or a **1** (i.e. we “don’t care” which)
- That is, it is **unspecified**,  
usually because of invalid inputs
- In K-Maps, “Don’t Cares” Can Be Advantageous!!

# Example of a Don't Care Situation

- Consider coding all decimal digits (say, for a digital clock app):
  - 0 thru 9 --- requires how many bits?
    - 4 bits
  - But! 4 bits convey more numbers than that!
    - Don't forget A thru F!
- Not all binary values map to decimal



## Example Continued...

Binary	Decimal
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7

Binary	Decimal
1000	8
1001	9
1010	X
1011	X
1100	X
1101	X
1110	X
1111	X

# Don't Care: So What?

---

- Recall that in a K-map, we can only group 1s
- Because the value of a don't care is irrelevant, we can treat it as a 1 ***if it is convenient to do so*** (or a 0 if that would be more convenient)

# Example

- A circuit that calculates if the 4-bit binary coded *single digit* decimal **input % 2 == 0**
- So, although 4-bits will give me numbers from 0 to 15, I *don't care* about the ones that yield 10 to 15.

I3	I2	I1	I0	R
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X



## Example as a K-Map

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	0	1
	01	1	0	0	1
	11	X	X	X	X
	10	1	0	X	X




If We **DO** Exploit “Don’t Cares”

$$R = \bar{I}_0$$

$I_1 I_0$		00	01	11	10
$I_3 I_2$					
00		1	0	0	1
01		1	0	0	1
11		X	X	X	X
10		1	0	X	X
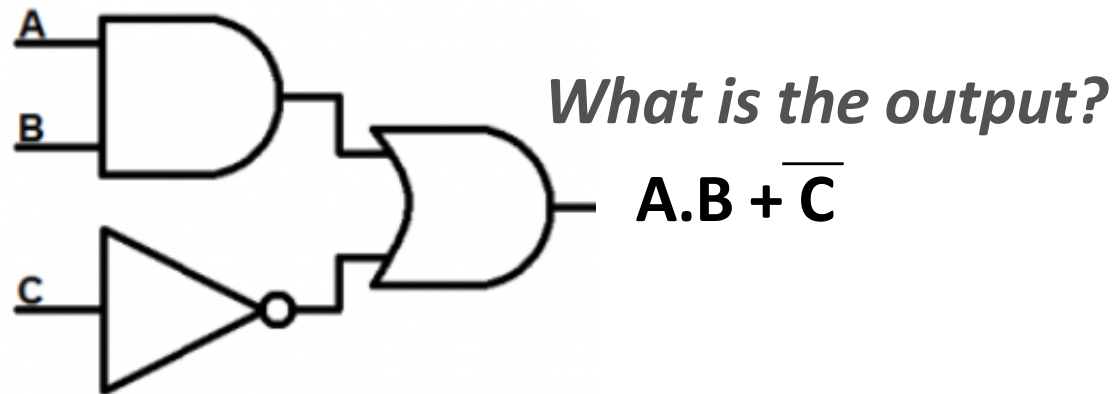
# Combinatorial Logic Designs

- When you *combine* multiple logic blocks together to form a more complex logic function/circuit



What is its truth table?

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

What is its K-Map?

		AB			
		00	01	11	10
C	0	1	1	1	1
	1			1	

# Exercise 1

- Given the following truth table, draw the resulting logic circuit
  - STEP 1:** Draw the K-Map and simplify the function
  - STEP 2:** Construct the circuit from the now simplified function

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Exercise 1 – Step 1  
*Get the simplified function*

		AB			
		00	01	11	10
CD	00		1	1	
	01				
	11			1	1
	10			1	1


$B = 1$  (grouping 01 and 11 for CD=00)  
 $A = 1$  (grouping 11 and 10 for CD=00, 11, 10)  
 $D = 1$  (grouping 01 and 11 for CD=11, 10)  
 $C = 1$  (grouping 01 and 11 for CD=11, 10)

$$F(A,B,C) = B.C'.D' + A.C$$

## Exercise 1 – Step 2

*Draw the logic circuit diagram*

$$F(A,B,C) = B.C'.D' + A.C$$

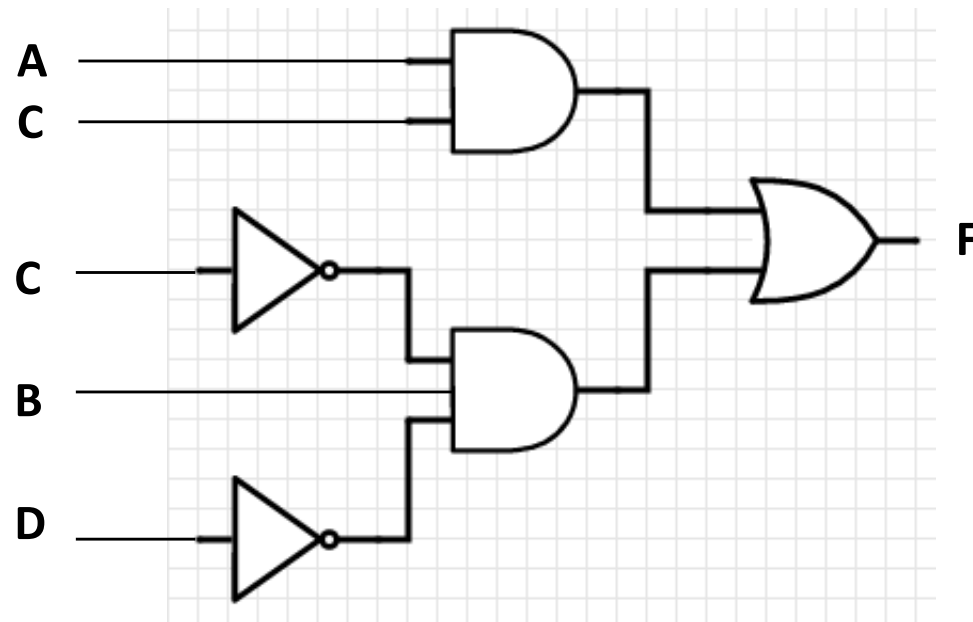



## Exercise 2

- Given the following truth table, draw the resulting logic circuit


A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

AB

C


	00	01	11	10
0	1	1		1
1	1			1

$$F(A,B,C) = B' + A'.C'$$

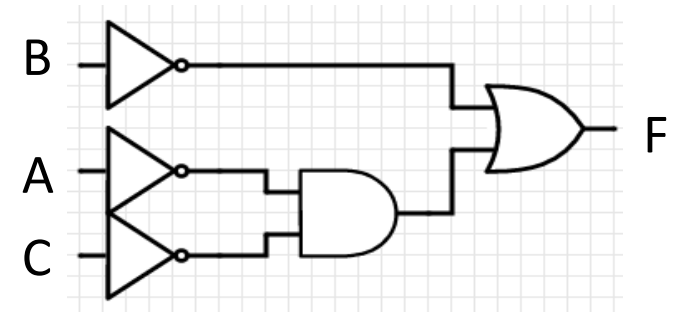
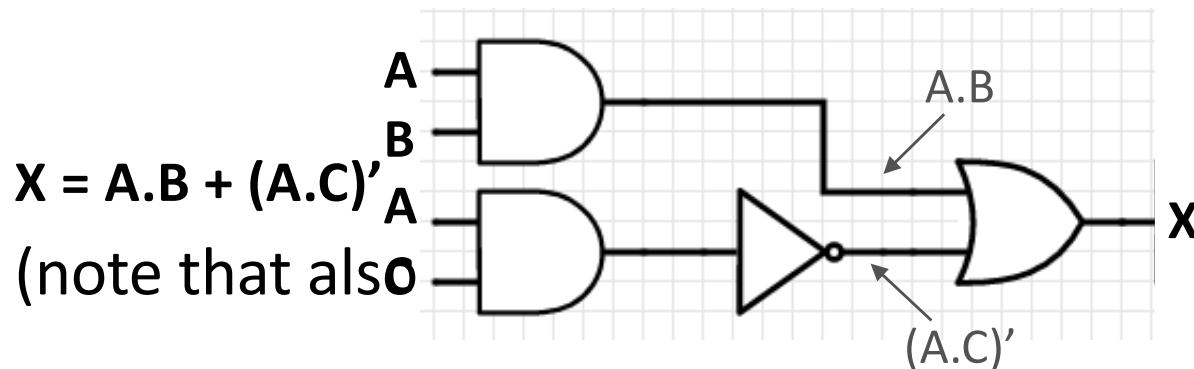
## Exercise 3


- Given the following schematic of a circuit, (a) write the function and (b) fill out the truth table:



A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	
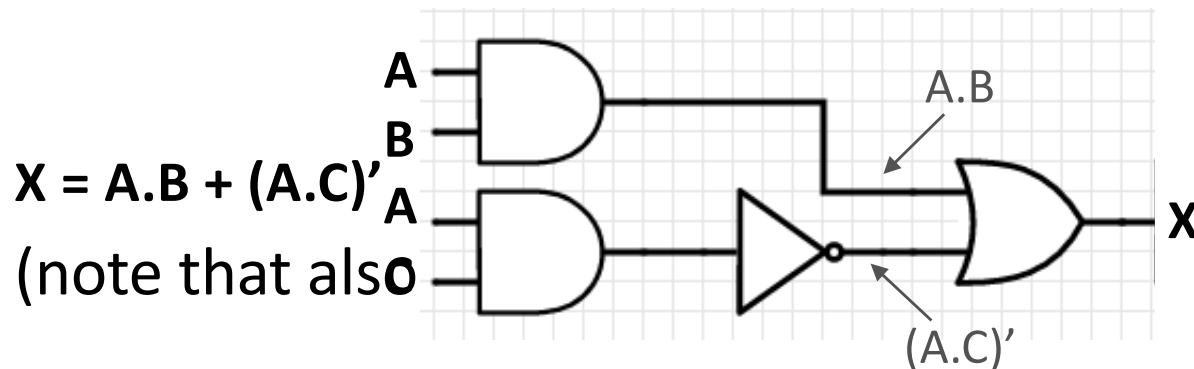
## Exercise 3

- Given the following schematic of a circuit, (a) write the function and (b) fill out the truth table:



A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

# Multiplexer

---


- A logical selector:
  - Select either input A or input B to be the output

```
// if s = 0, output is a
// if s = 1, output is b
int mux(int a, int b, int s)
{
    if (!s) return a;
    else return b;
}
```
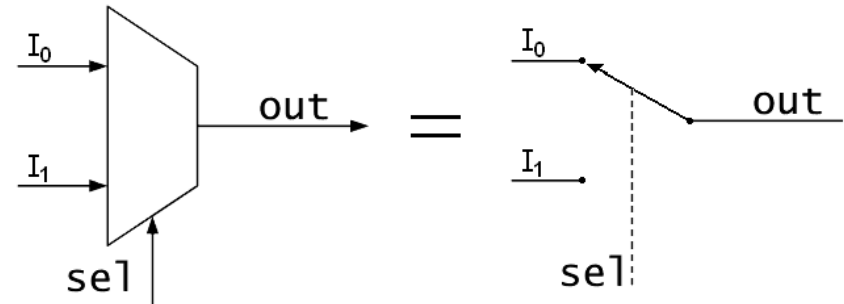
# Multiplexer

(Mux for short)

- Typically has 3 *groups of* inputs and 1 output
  - IN: 2 data , 1 select
  - OUT: 1 data



- 1 of the input data lines gets selected to become the output, based on the 3<sup>rd</sup> (select) input
  - If “Sel” = 0, then  $I_0$  gets to be the output
  - If “Sel” = 1, then  $I_1$  gets to be the output
- The opposite of a Mux is called a **Demultiplexer** (or **Demux**)



# Mux Truth Table and Logic Circuit

## 1-bit Mux

$I_0$	$I_1$	$S$	$O$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$S$	$I_0 \ I_1$			
	00	01	11	10
0			1	1
1		1	1	

$$O = S \cdot I_1 + S' \cdot I_0$$

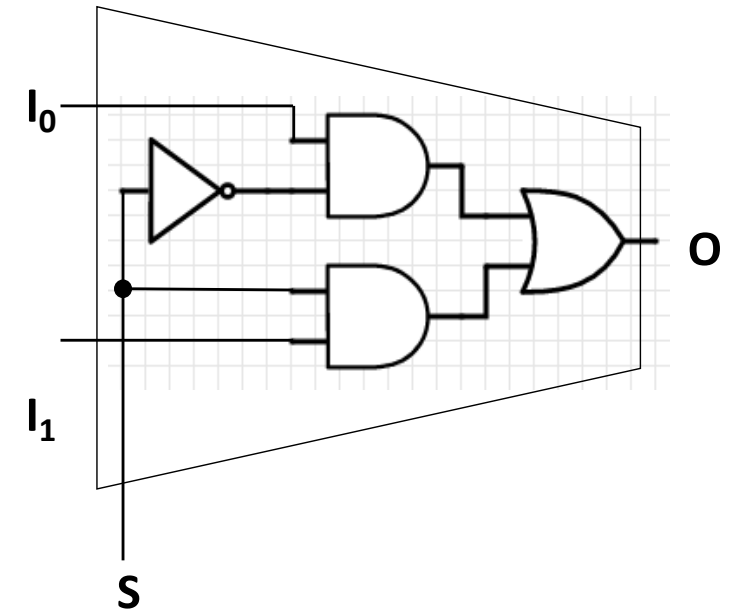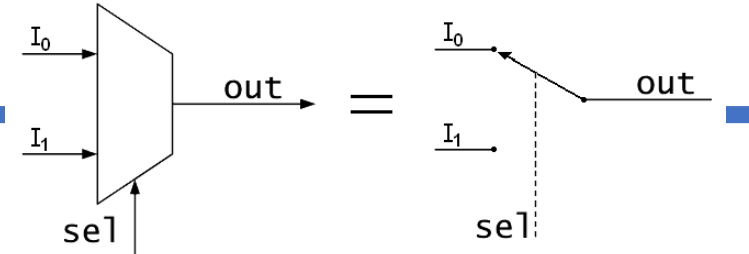

• = lines are physically connected

# YOUR TO-DOs

---


- Lab 6!

**</LECTURE>**



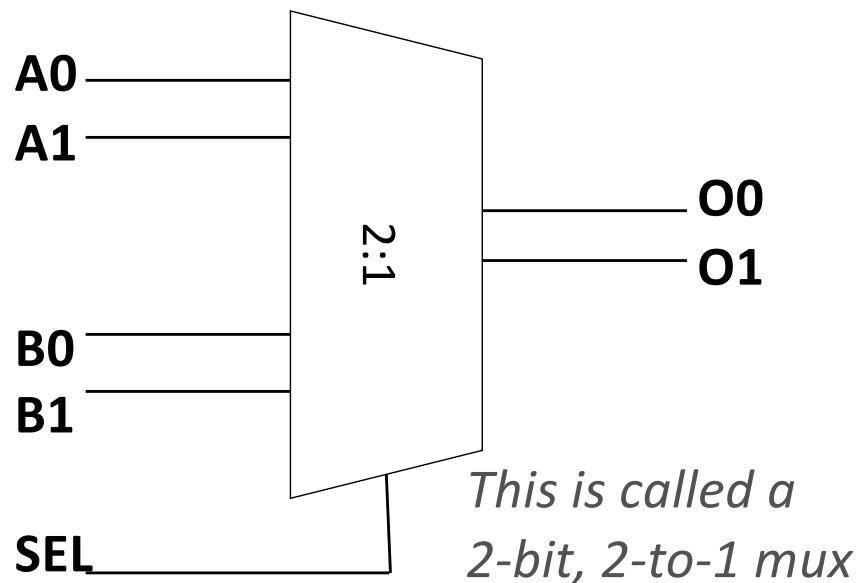
# Mux Configurations

Muxes can have I/O that are multiple bits




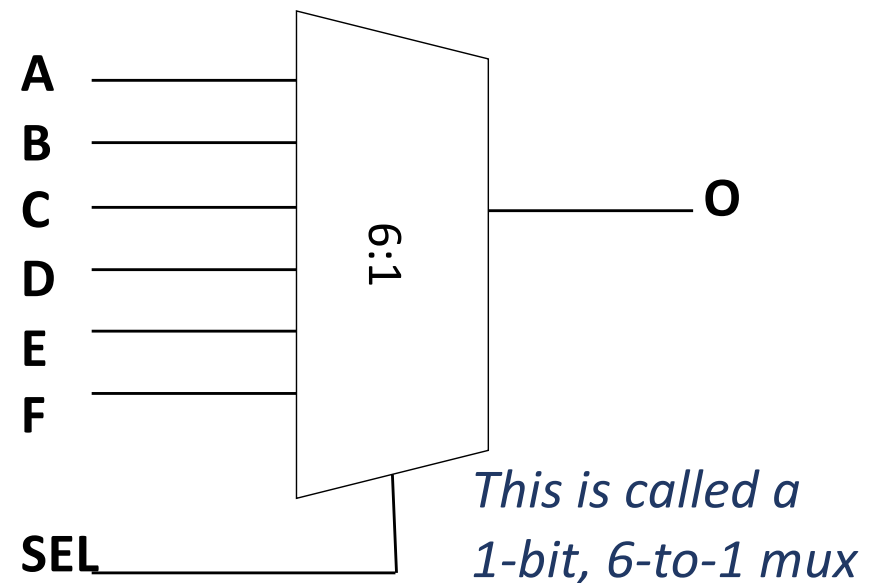Or they can have more than two data inputs



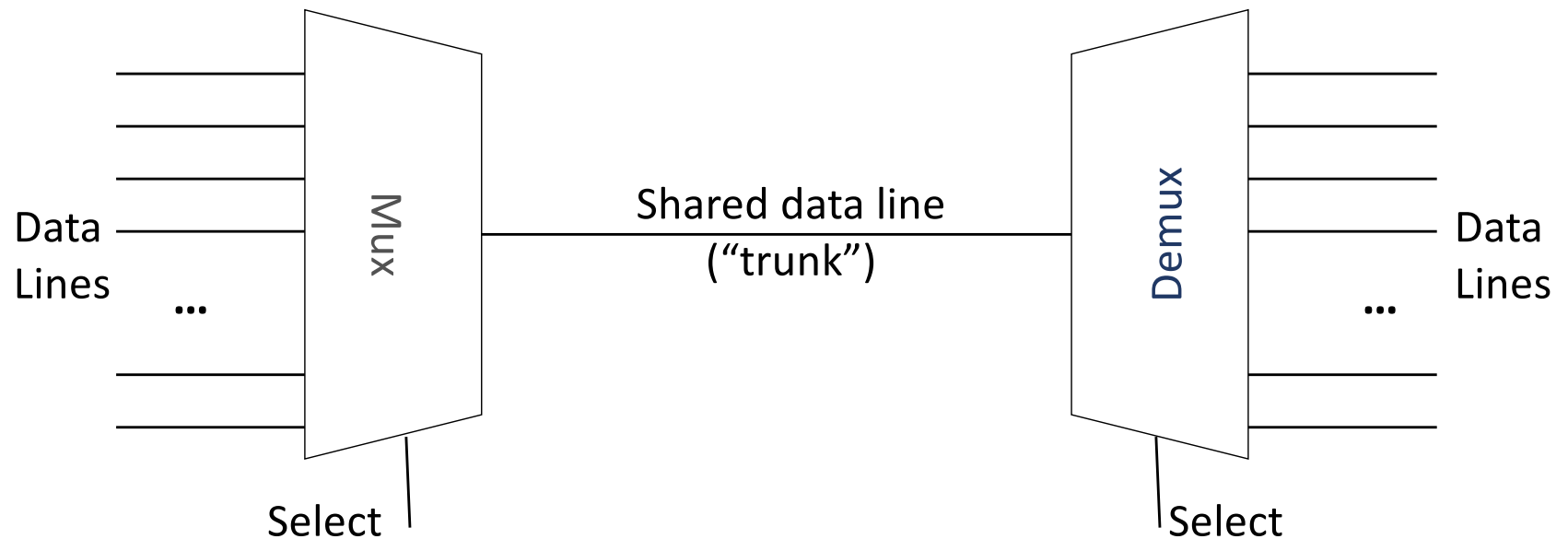
# The Use of Multiplexers

- Makes it possible for several signals (variables) to share one resource
  - Very commonly used in data communication lines



# Selection Lines in Muxes

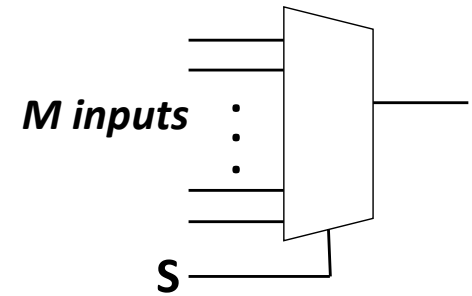

- General mux description: **N-bit, M-to-1**
- Where:            N = how “wide” the input is (# of input bits, min. 1)  
                      M = how many inputs to the mux (min. 2)
- The “select” input (S) has to be able to select **1 out of M inputs**
  - So, if  $M = 2$ ,    S should be at least 1 bit    *(S = 0 for one line, S = 1 for the other)*
  - But if  $M = 3$ ,    S should be at least **2 bits**    *(why?)*
  - If  $M = 4$ ,                            S should be ???    *(ANS: at least 2 bits)*
  - If  $M = 5$ ,                            S should be ???    *(ANS: at least 3 bits)*

# Combining Muxes Together

---

Can I do a **4:1** mux from 2:1 muxes?

Generally, you can do  **$2^n$ :1** muxes from 2:1 muxes.